

Student's Name:

### Introduction to circuit analysis

#### *Homework 2 – Basic Circuit Terminology and basic laws*

#### Instructions:

- You have to show all work in order to receive full credit
  - All answer must be in engineering notation rounded off to the hundredth
- 

1. Convert 0.0003697581 km to mm (millimeters)
2. Convert 13623.58  $\Omega$  to k $\Omega$
3. Given the voltage formula  $V = \frac{w}{q}$  If the potential energy between two points is 12.5 V, how much energy is expected to bring 750.8 mC from one point to the other?

For question 4 and 5. Given the current formula  $I = \frac{Q}{t}$

4. If a current of 18.75 mA exists for 2.25 hours in a wire, how many coulombs of charge have passed through the wire?
5. How many minutes will a charge of 22.662 mC passes through a light bulb if the current is constant at 125.9  $\mu$ A

### **Ohm's Law**

6. What is the current through a  $2.2\Omega$  resistor if the voltage drop across it is 24 V?
7. If a voltmeter has an internal resistance of  $50\text{ k}\Omega$  find the current through the meter when it reads 120 V.
8. In a TV camera, a current of 5.6 mA passes through a resistor of  $3.3\text{ M}\Omega$  What is the voltage drop across the resistor?

### **Power Law**



9. The power consumed by a  $2.2\text{ k}\Omega$  resistor is 240 mW. What is the current level through the resistor?
10. A  $2.2\text{ k}\Omega$  resistor in a stereo system dissipates 42 mW of power. What is the voltage across the resistor?

11. What are the “hot” resistance level and current rating of a 120 V, 100 W bulb?


12. What is the power delivered by a 12 V battery if the current drain is 40 A?

### Kirchhoff's Laws

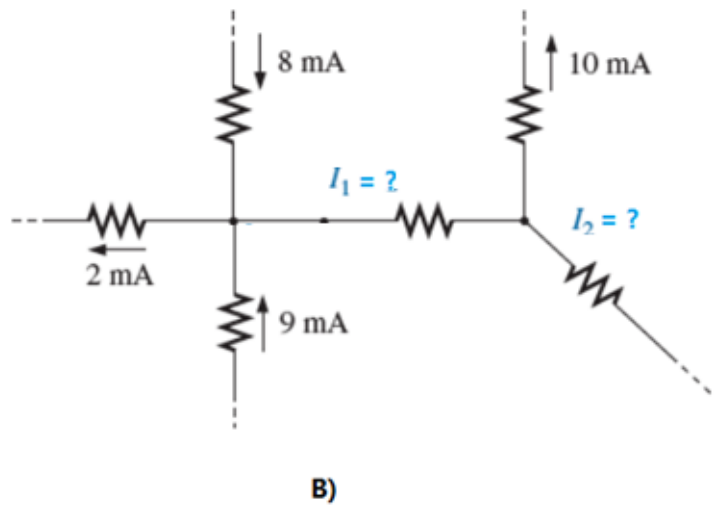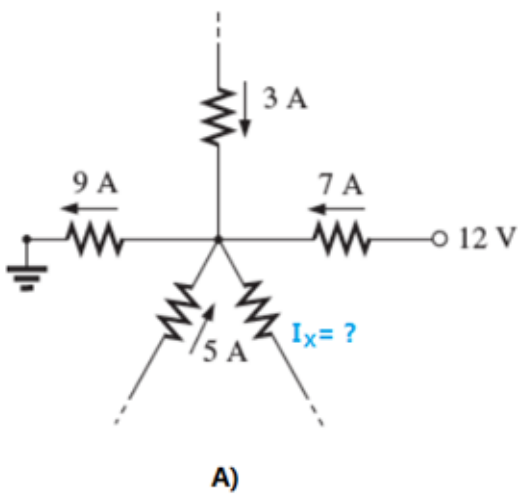13. Use Kirchhoff's Current Law (KCL) to find the unknown current




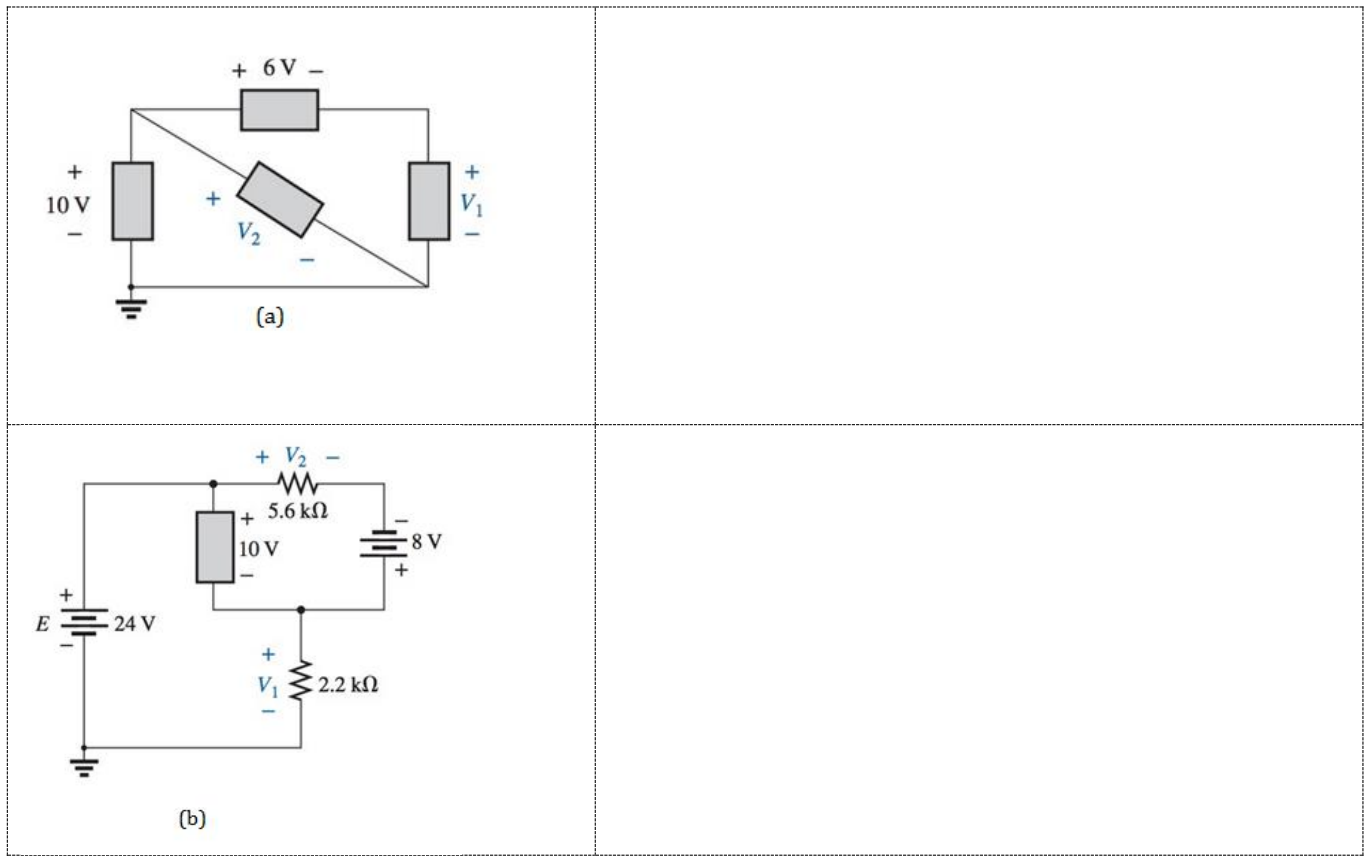14. Use Kirchhoff's Voltage Law (KVL) to find the unknown voltage



### Circuit Terminologies

15. For the following circuit,

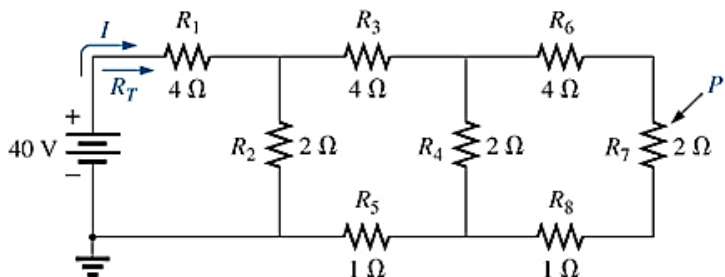

The number of independent loops is: \_\_\_\_\_

The number of elements is: \_\_\_\_\_

The number of nodes is: \_\_\_\_\_

16. In your own words, what is direct current (dc) and alternating current (ac) \_\_\_\_\_

---



---



---



---

**Multiple Choices Questions (Circle only ONE correct answer)**

17. If an element permits a generous flow of electrons with very little external force is known as \_\_\_\_\_ and if it does not permit a generous flow of electrons is known as \_\_\_\_\_.

- a) Insulator, conductor
- b) Conductor, insulator
- c) Conductor, semiconductor
- d) Insulator, semiconductor
- e) Conductor, conductor

18. A voltage source is:

- a. A passive element
- b. An active element
- c. An independent source
- d. A dependent source
- e. A sinewave

19. A resistor is:

- a. A passive element
- b. An active element
- c. An independent source
- d. A dependent source
- e. A sinewave

20. The following electronics symbols is:



- a. A dc current source
- b. An ac current source
- c. A dc voltage source
- d. An ac voltage source
- e. A dc-ac current source
- f. A dc-ac voltage source

----- **Homework Ends Here** -----