

Student's Name:

Introduction to Circuit Analysis


Homework 8 – Thevenin's, MPT, and Norton theorem

Instructions:

- You have to show all work in order to receive full credit
- All answer must be in engineering notation rounded off to the hundredth


Question 1) For the following circuit below:

- Determine the Thevenin's equivalent circuit (15 pts)
- Using the Thevenin's equivalent circuit, determine the load resistor if the load voltage drop through it is 10 V (5 pts)
- Using the Thevenin's equivalent circuit, find the maximum power transfer to R_{Load} (5 pts)
- Using the Thevenin's equivalent circuit, find the Norton equivalent circuit (5 pts)

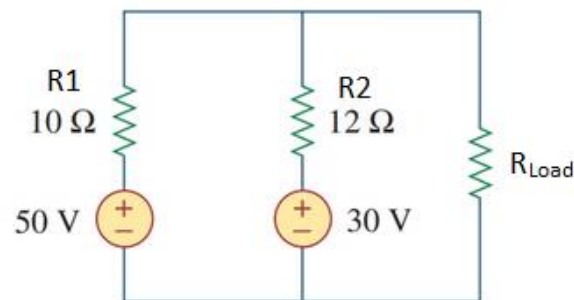

Question 2) For the following circuit, assuming that R_3 is the load resistor,

- Find the Thevenin's equivalent circuit for the load resistor R_3 (15 pts)
- According to the Thevenin's equivalent circuit, what will be the voltage through load resistor if $R_L = 5 \Omega$? (5 pts)
- Using the Thevenin's equivalent circuit, determine the load resistor if the load voltage drop through it is 10 V (5 pts)
- According to the Thevenin's equivalent circuit, what will be the maximum power transfer through load resistor? (5 pts)
- According to the Thevenin's equivalent circuit, find the Norton equivalent circuit (5pts)

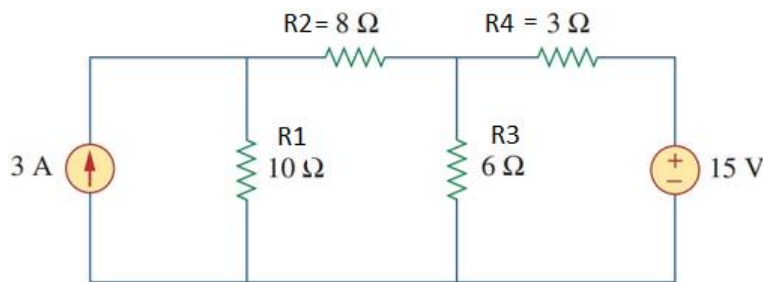

Question 3) For the following circuit below:

- Determine the Thevenin's equivalent circuit (15 pts)
- Using the Thevenin's equivalent circuit, determine the voltage through the load resistor $R_L = 10\ \Omega$ (5 pts)
- Using the Thevenin's equivalent circuit, determine the load resistor if the load voltage drop through it is 8 V (5 pts)
- According to the Thevenin's equivalent circuit, find the maximum power transfer to R_L (5 pts)
- According to the Thevenin's equivalent circuit, find the Norton equivalent circuit (5 pts)

