

Student's Name:

Introduction to circuit analysis
Basic laws, series, parallel, series-parallel circuit


Instructions:

- You have to show all work in order to receive full credit
 - All answer must be in engineering notation rounded off to the hundredth
-

Multiple choices: circle only ONE answer

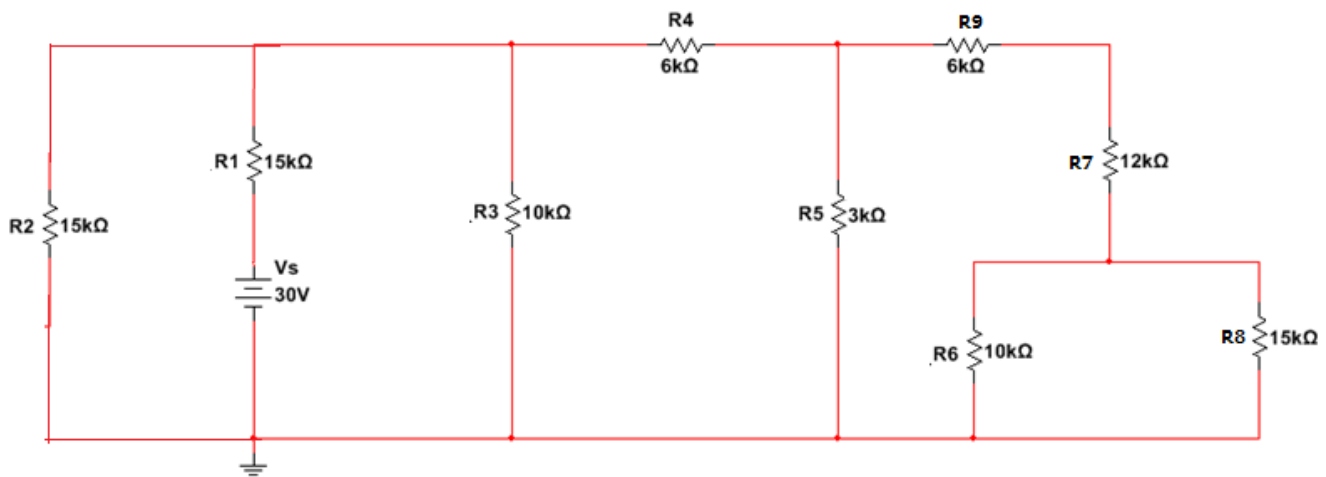Question 1

For the following network: (0.3 pts each)



Which resistor will have **30 V** drop?

- None of them
- R_5
- R_6
- R_3
- R_1
- R_2

Which of the following resistors share **the same current**?


- R_8 and R_9
- R_2 and R_3
- R_1 and R_2
- R_3 and R_4
- R_9 and R_7
- None of them

Which of the following resistors share **the same voltage**?

- R_1 and R_2
 - R_6 and R_8
 - R_7 and R_8
 - R_5 and R_7
 - R_1 and R_3
 - None of them
-

Question 2


For the following circuit, solve for:

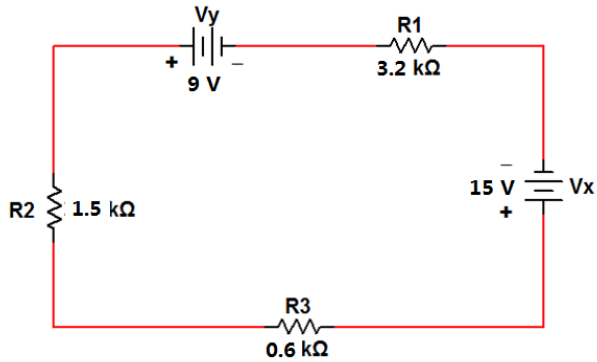

- Current source (0.8 pts) _____
- Indicate the direction of the current flow (clockwise or counterclockwise) (0.2 pts) _____
- Voltage drop in R_1 , V_{R1} , and indicate the polarity (+, -) (0.4 pts) _____
- Voltage drop in R_2 , V_{R2} , and indicate the polarity (+, -) (0.4 pts) _____
- Voltage drop in R_3 , V_{R3} , and indicate the polarity (+, -) (0.4 pts) _____

Question 3


For the following circuit, solve for:

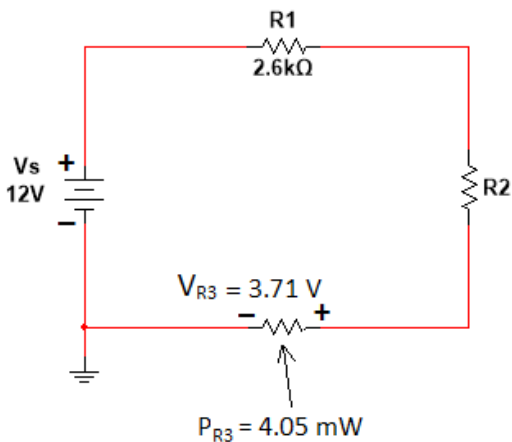

- Current source (0.6 pts) _____
- Indicate the direction of the current flow (clockwise or counterclockwise) (0.2 pts) _____
- Voltage across R_1 (with polarity) (0.4 pts) _____
- Resistor R_2 , (0.6 pts) _____

Question 4


For the following circuit, solve for:

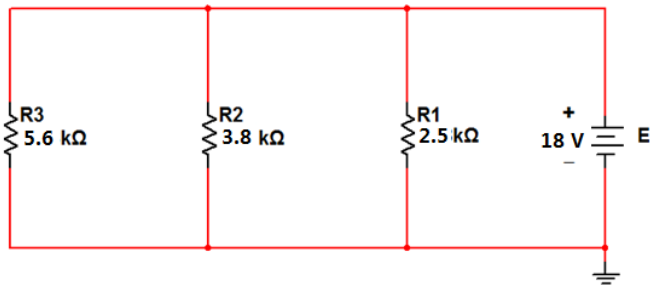

- a. Total resistance, R_T (0.6 pts) _____
- b. The current through R_1 , I_{R1} (0.3 pts) _____
- c. The current through R_2 , I_{R2} (0.3 pts) _____
- d. The current through R_3 , I_{R3} (0.3 pts) _____
- e. The total current, I_T (0.3 pts) _____

Question 5


For the following circuit, find:

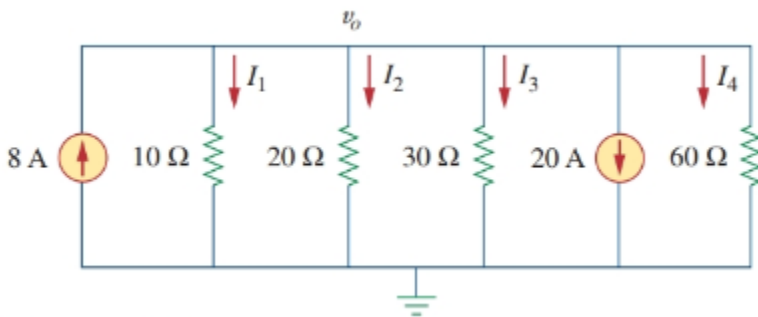

- a. (0.6 pts) Total resistance _____
- b. (0.3 pts) Total current source _____
- c. (0.3 pts) Total voltage source _____
- d. (0.35 each pts) The current through each resistor
 I_1 _____ I_2 _____
 I_3 _____ I_4 _____

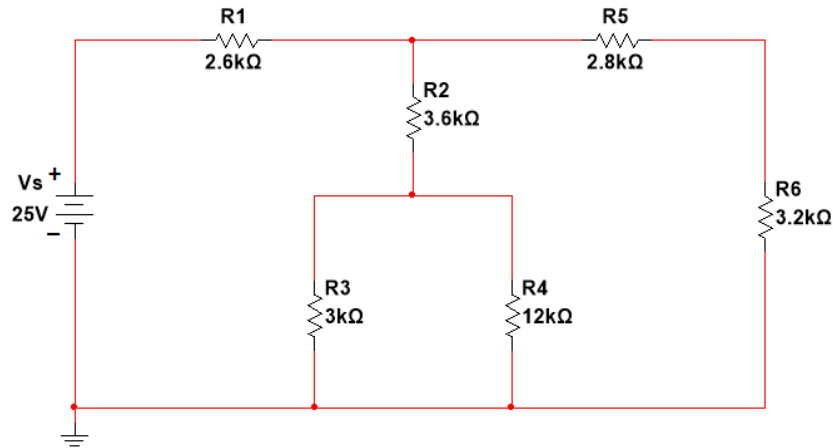Question 6

For the following series-parallel circuit, find



- Sketch three equivalent circuit (0.9 pts → 0.3 pts each)
- Total resistance, R_T (1 pts) _____
- (0.6 pts) Voltage in R_1 , V_{R1} _____, current in R_1 , I_{R1} _____
- (0.65 pts) Voltage in R_2 , V_{R2} _____, current in R_2 , I_{R2} _____
- (0.6 pts) Voltage in R_3 , V_{R3} _____, current in R_3 , I_{R3} _____
- (0.6 pts) Voltage in R_4 , V_{R4} _____, current in R_4 , I_{R4} _____
- (0.7 pts) Voltage in R_5 , V_{R5} _____, current in R_5 , I_{R5} _____
- (0.7 pts) Voltage in R_6 , V_{R6} _____, current in R_6 , I_{R6} _____

----- Homework Ends Here -----