

Student's Name:


## Introduction to circuit analysis

### Homework 3 – Series dc circuit


#### Instructions:

- You have to show all work in order to receive full credit
- All answer must be in engineering notation rounded off to the hundredth

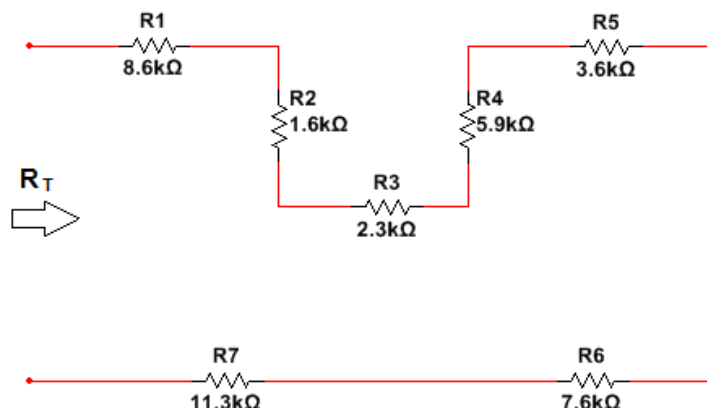1. Find the total resistance  $R_T$  of a given circuit (8 pts)




2. For the series configuration circuit

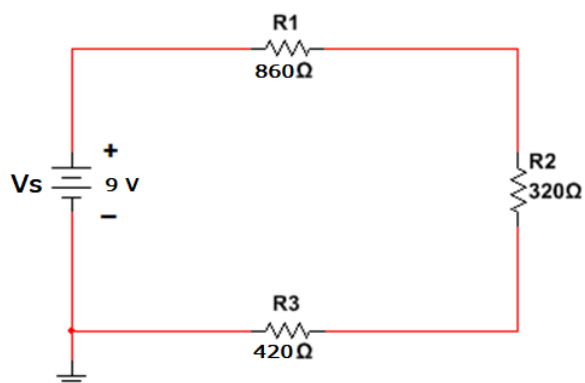

- Find the total resistance (7 pts) \_\_\_\_\_
- Calculate the source current (3 pts) \_\_\_\_\_
- Find the voltage across each resistor (7 pts)  
 $V_{R1}$  \_\_\_\_\_  $V_{R2}$  \_\_\_\_\_  $V_{R3}$  \_\_\_\_\_
- Calculate power dissipated by the source (3 pts) \_\_\_\_\_
- Calculate power dissipated by each resistor (7 pts):  
 $P_{R1}$  \_\_\_\_\_  $P_{R2}$  \_\_\_\_\_  $P_{R3}$  \_\_\_\_\_

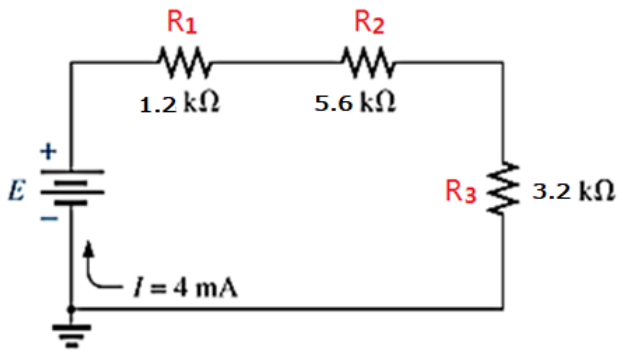
3. Find the voltage source value,  $E$ , that will result in the given current (7 pts) \_\_\_\_\_



(3 pts) Find  $P_{R1}$  \_\_\_\_\_

(3 pts) Find  $P_T$  \_\_\_\_\_

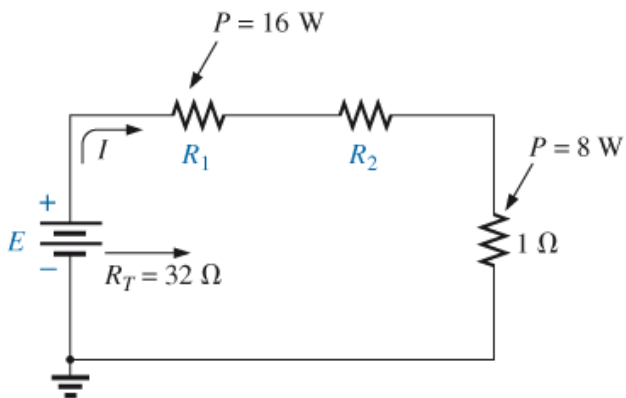4. Using the provided information, find the unknown quantities for  $E$ ,  $V_1$ ,  $V_2$ ,  $V_3$ ,  $R_1$ , and  $R_2$




(3 pts)  $E$  \_\_\_\_\_ (3 pts)  $V_1$  \_\_\_\_\_


(3 pts)  $V_2$  \_\_\_\_\_ (3 pts)  $V_3$  \_\_\_\_\_

(4 pts)  $R_2$  \_\_\_\_\_

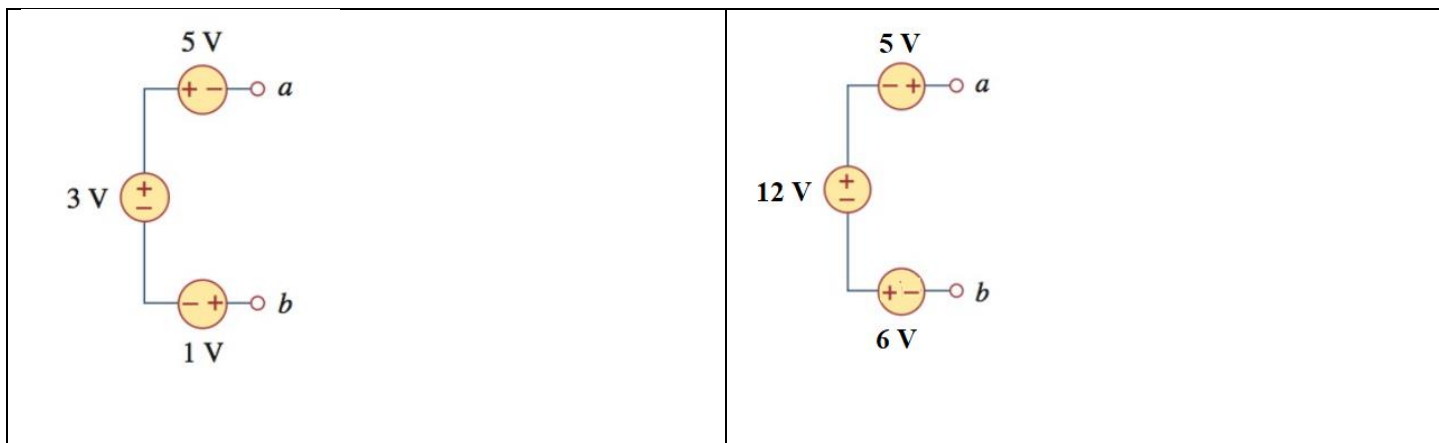5. Find the equivalent or total voltage for each of the following circuit (3 pts each):




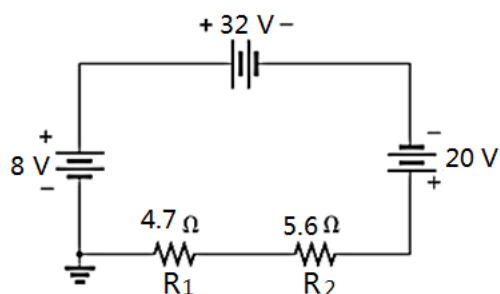6. For the following circuits, determine the current direction and value of the circuit, and the voltage drop through each resistor with their respective voltage polarities:



$I_{\text{equivalent}} = \underline{\hspace{2cm}}$  (9 pts) (clockwise or counterclockwise)

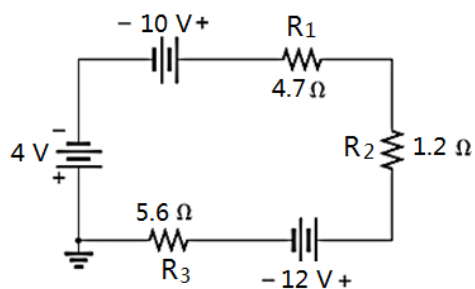$V_{R1} \underline{\hspace{2cm}}$  (3 pts)     $V_{R2} \underline{\hspace{2cm}}$  (3 pts)



$I_{\text{equivalent}} = \underline{\hspace{2cm}}$  (clockwise or counterclockwise) (9 pts)

$V_{R1} \underline{\hspace{2cm}}$  (3 pts)     $V_{R2} \underline{\hspace{2cm}}$  (3 pts)     $V_{R3} \underline{\hspace{2cm}}$  (3 pts)

-----HOMEWORK ENDS HERE -----