

ET 110 – Circuit Analysis

Homework 5 – Basic laws, series, parallel, series-parallel circuit

Student's Name: _____

Instructions:


- Due date: _____
- Total of 15 extra points
- YOU HAVE TO SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT
- All answer must be in engineering notation rounded off to the hundredth

----- Homework Starts Here -----

Multiple choices: circle only ONE answer

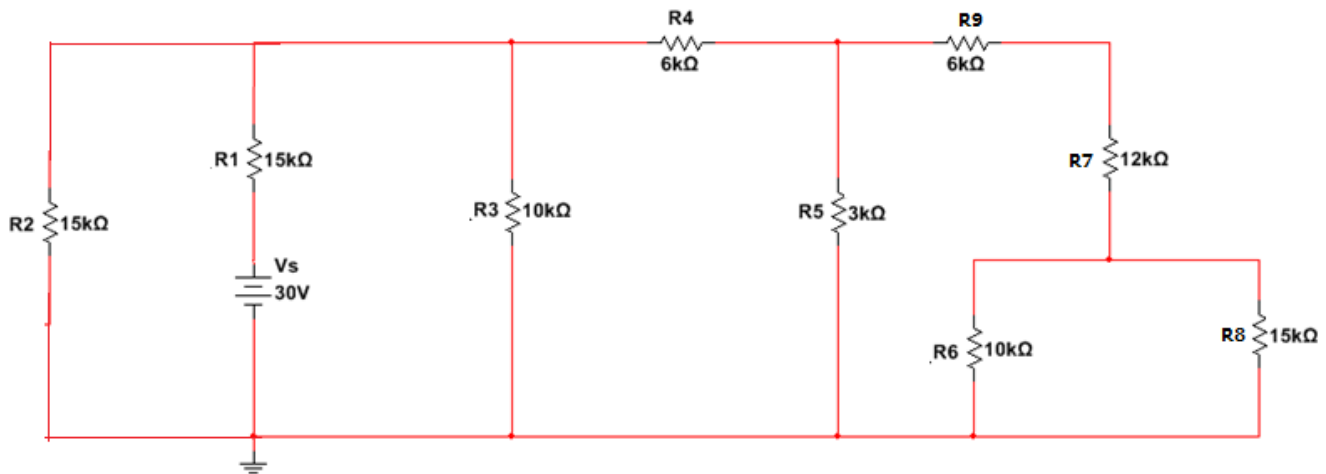Question 1

For the following network: (0.3 pts each)



Which resistor will have **30 V** drop?

- None of them
- R5
- R6
- R3
- R1
- R2

Which of the following resistors share *the same current*?


- R8 and R9
- R2 and R3
- R1 and R2
- R3 and R4
- R9 and R7
- None of them

Which of the following resistors share *the same voltage*?

- R1 and R2
 - R6 and R8
 - R7 and R8
 - R5 and R7
 - R1 and R3
 - None of them
-

Question 2


For the following circuit, solve for:

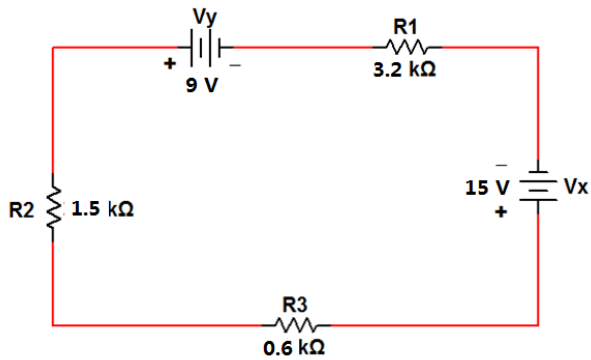

- Current source (0.8 pts) _____
- Indicate the direction of the current flow (clockwise or counterclockwise) (0.2 pts) _____
- Voltage drop in R_1 , V_{R1} , and indicate the polarity (+, -) (0.4 pts) _____
- Voltage drop in R_2 , V_{R2} , and indicate the polarity (+, -) (0.4 pts) _____
- Voltage drop in R_3 , V_{R3} , and indicate the polarity (+, -) (0.4 pts) _____

Question 3


For the following circuit, solve for:

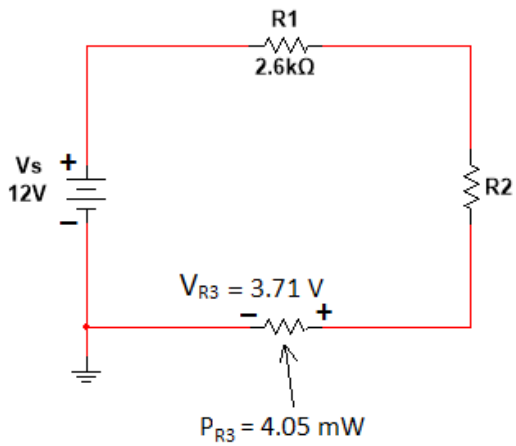

- Current source (0.6 pts) _____
- Indicate the direction of the current flow (clockwise or counterclockwise) (0.2 pts) _____
- Voltage across R_1 (with polarity)(0.4 pts) _____
- Resistor R_2 , (0.6 pts) _____

Question 4


For the following circuit, solve for:

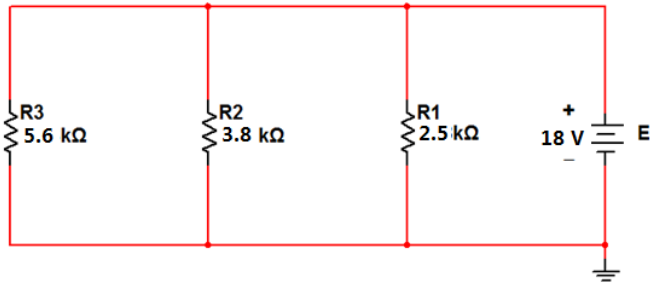

- Total resistance, R_T (0.6 pts) _____
- The current through R_1 , I_{R1} (0.3 pts) _____
- The current through R_2 , I_{R2} (0.3 pts) _____
- The current through R_3 , I_{R3} (0.3 pts) _____
- The total current, I_T (0.3 pts) _____

Question 5

For the following circuit, find:

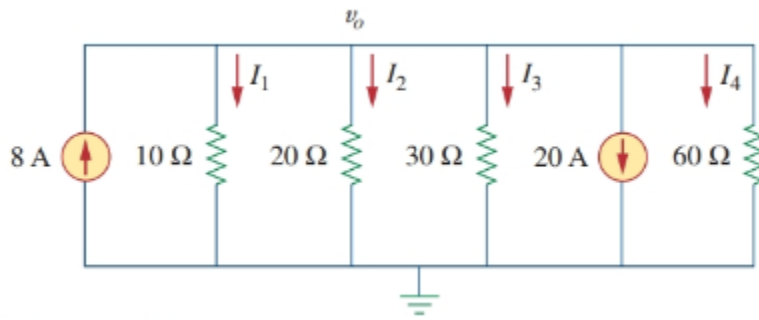

a. (0.6 pts) Total resistance _____

b. (0.3 pts) Total current source _____

c. (0.3 pts) Total voltage source _____


d. (0.35 each pts) The current through each resistor

I_1 _____ I_2 _____

I_3 _____ I_4 _____

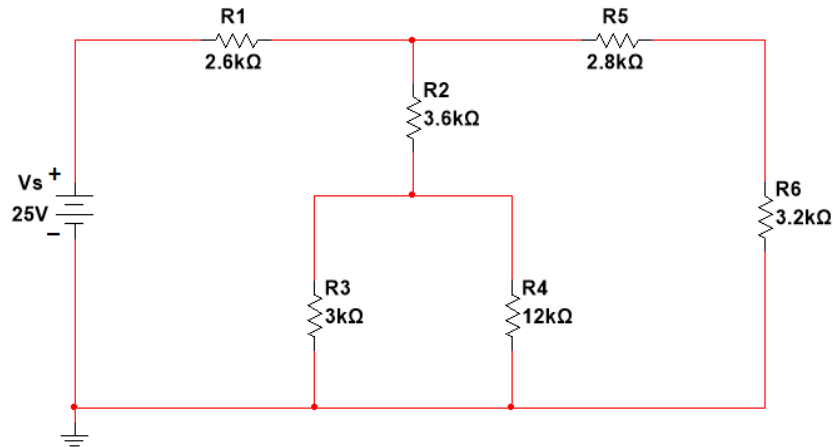Question 6

For the following series-parallel circuit, find



- Sketch three equivalent circuit (0.9 pts → 0.3 pts each)
- Total resistance, R_T (1 pts) _____
- (0.6 pts) Voltage in R_1 , V_{R1} _____, current in R_1 , I_{R1} _____
- (0.65 pts) Voltage in R_2 , V_{R2} _____, current in R_2 , I_{R2} _____
- (0.6 pts) Voltage in R_3 , V_{R3} _____, current in R_3 , I_{R3} _____
- (0.6 pts) Voltage in R_4 , V_{R4} _____, current in R_4 , I_{R4} _____
- (0.7 pts) Voltage in R_5 , V_{R5} _____, current in R_5 , I_{R5} _____
- (0.7 pts) Voltage in R_6 , V_{R6} _____, current in R_6 , I_{R6} _____

----- **Homework Ends Here** -----