



Student's Name: _____

Introduction to circuit analysis
Homework # 5 – Series-Parallel dc circuit


Instructions:

- You have to show all work in order to receive full credit
- All answer must be in engineering notation rounded off to the hundredth

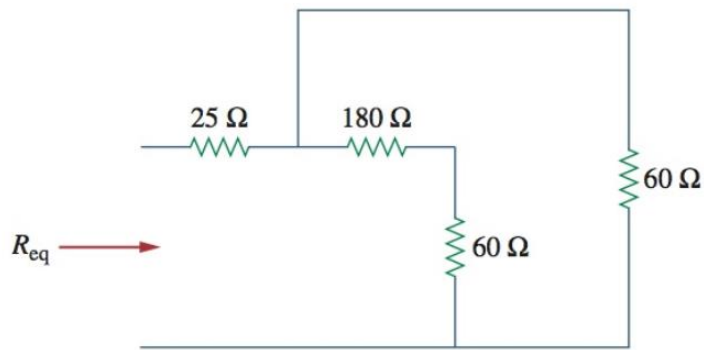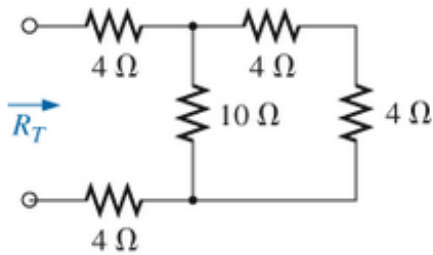1) Determine the total resistance, R_T (3 pts)



2) For the following circuit:

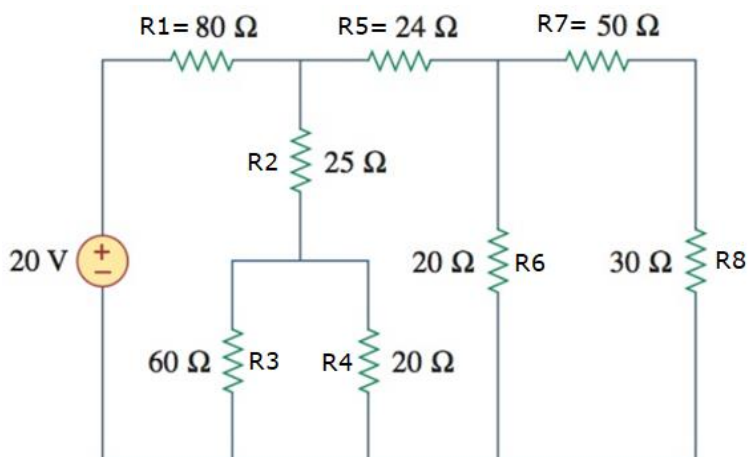

- Sketch 3 equivalent circuit (3 pts)
- (6 pts) Find the total resistance, R_T _____
- (2 pts) Calculate I_T or I_S _____

Find the voltage across each resistor (2 pts each)

V_{R1} _____

V_{R2} _____

V_{R3} _____

V_{R4} _____

V_{R5} _____

V_{R6} _____

V_{R7} _____

V_{R8} _____

Find the current through each resistor (2 pts each)

I_{R1} _____

I_{R2} _____

I_{R3} _____

I_{R4} _____


I_{R5} _____

I_{R6} _____

I_{R7} _____

I_{R8} _____

3) For the ladder network

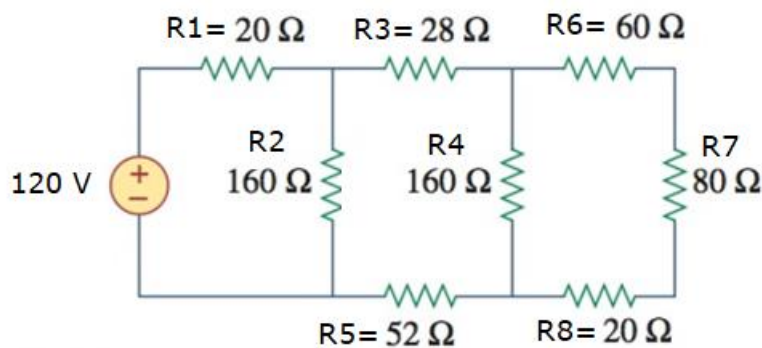

a. Sketch three equivalent circuit (3pts)

b. (8 pts) Determine R_T _____

c. (2 pts) Calculate I_S _____

Find the voltage across each resistor (2 pts each)

V_{R1} _____

V_{R2} _____

V_{R3} _____

V_{R4} _____

V_{R5} _____

V_{R6} _____

V_{R7} _____

V_{R8} _____

Find the current through each resistor (2 pts)

I_{R1} _____

I_{R2} _____

I_{R3} _____

I_{R4} _____

I_{R5} _____

I_{R6} _____

I_{R7} _____

I_{R8} _____

4) For the network

- a. (2 pts) Sketch two equivalent circuit
- b. (3 pts) Determine R_T
- b. (3 pts) Find I_{R1} , I_{R2} , and I_{R3}
- c. (3 pts) Find voltage V_{R1} , V_{R2} , and V_{R3}

