

Student's Name:


Introduction to circuit analysis

Homework 6 – Circuit theorems: source transformation and superposition


Instructions:

- You have to show all work in order to receive full credit
- All answer must be in engineering notation rounded off to the hundredth

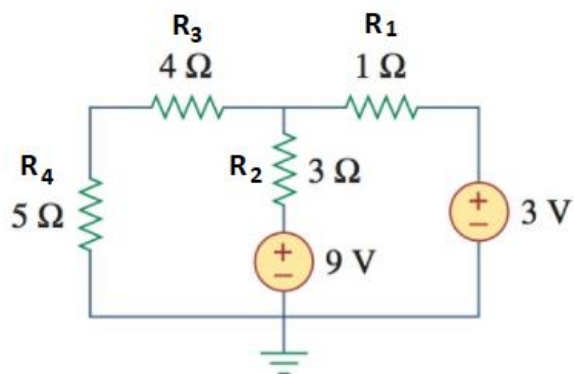
1) (28 pts) Use *superposition theorem* to the voltage across R_1



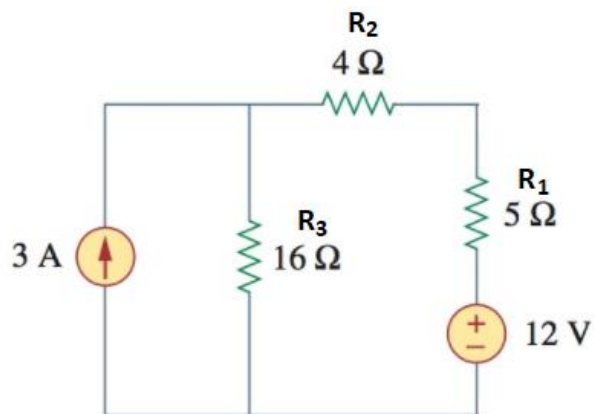
2) (28 pts) Use *superposition theorem* to the voltage across R_3



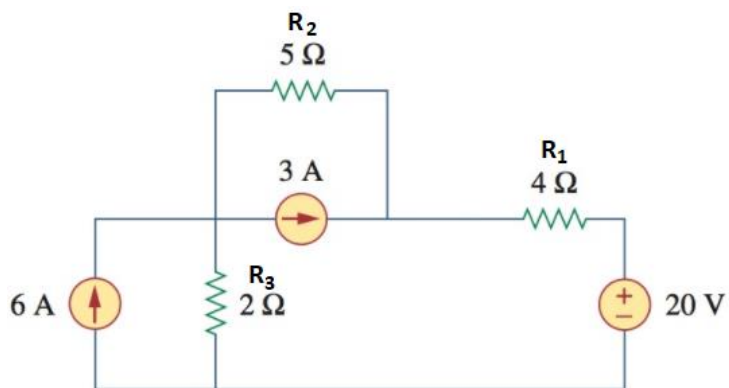3) (20 pts) Use *source conversion* to find the voltage across R_1



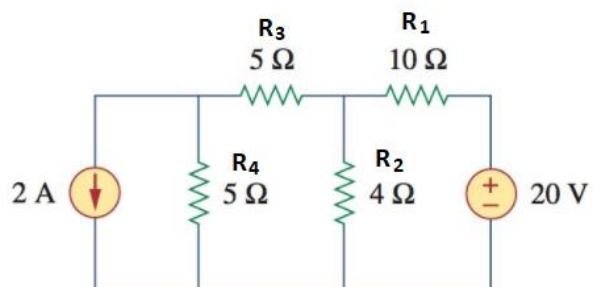4) (24 pts) Use *source conversion* to find the current through R_1



----- Homework Ends Here -----