
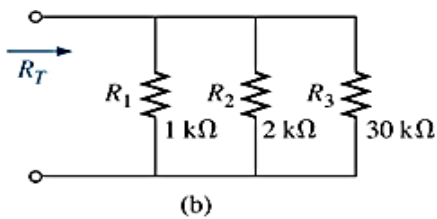


Introduction to circuit analysis
Homework 4 – Parallel dc circuit


Instructions:

- You have to show all work in order to receive full credit
- All answer must be in engineering notation rounded off to the hundredth

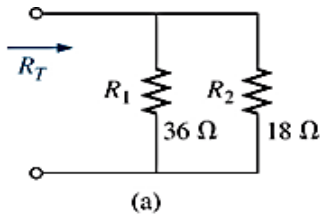1. Find the total resistance for each configuration parallel circuit (a = 8 pts, b = 10 pts)




2. For the following parallel circuit

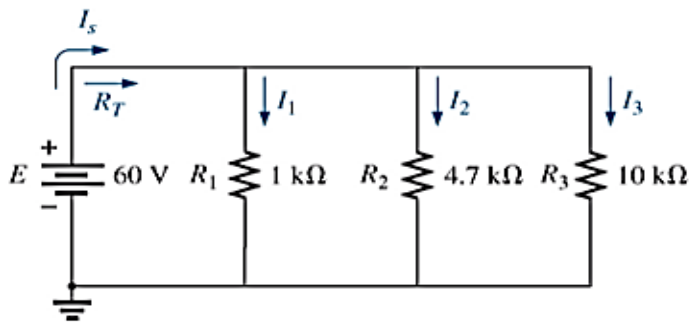

- Find the total resistance and the current through each branch (10 pts)
- Find the power delivered to each resistor (15 pts)
- Calculate the power delivered by the source (5 pts)

3. Find the unknown quantities for the following parallel circuit, (8.5 points each)

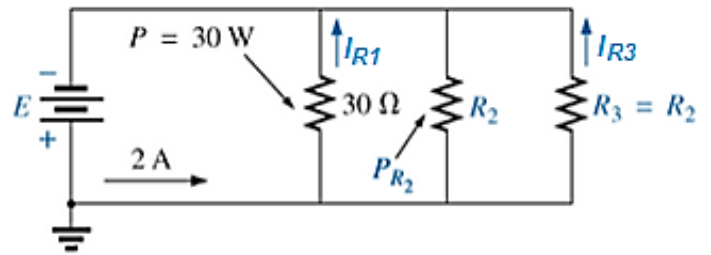- a. I_{R1} , current through $R1$ _____
- b. I_{R3} , current through $R3$ _____
- c. Resistance at $R2$ _____
- d. Resistance at $R3$ _____
- e. Power dissipation at $R2, P_{R2}$ _____
- f. Voltage source, E _____



-----HOMEWORK ENDS HERE -----